


Module 1 - Lesson 06: Logic Gates & Circuits

Logic Gates

An application of Boolean algebra is to model circuits inside electronic devices. All inputs and outputs within the devices can be thought of as switches that contain a value in the set $\{0, 1\}$. The 0 represents the switch being "off" and 1 represents the switch being "on". The circuits of an electronic device can be modelled using a series of elements called gates. The following points are important to understand.

- Electronic gates require a power supply.
- Gate **INPUTS** are driven by voltages having two nominal values, e.g. 0V and 5V representing logic 0 and logic 1 respectively.
- The **OUTPUT** of a gate provides two nominal values of voltage only, e.g. 0V and 5V representing logic 0 and logic 1 respectively. In general, there is only one output to a logic gate
- There is always a time delay between an input being applied and the output responding.

Types of Gates

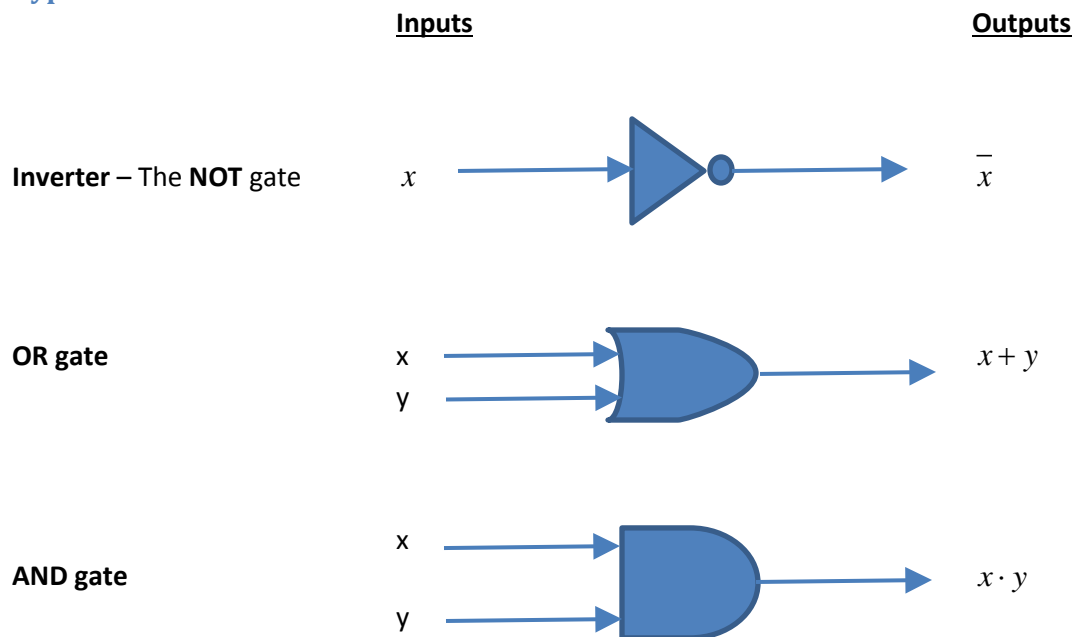


An **inverter** can only have one input and one output.


OR and **AND** gates have at least two inputs and one output.

Gates with n Inputs

OR gate

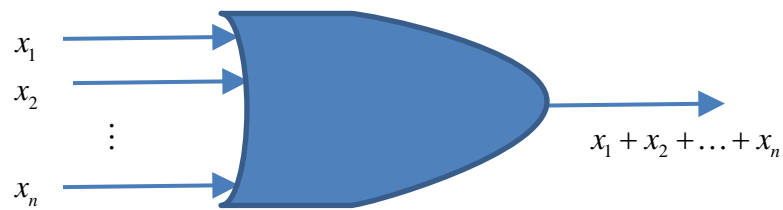

AND gate

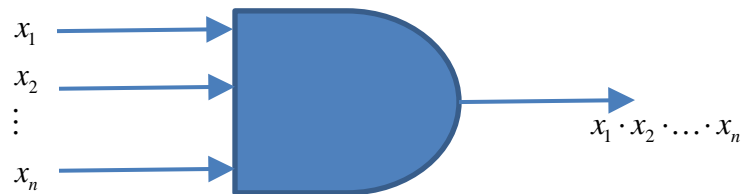

Constructing Circuits

When constructing circuits using gates, the inputs can be shared across all gates or each gate can have a separate set of inputs. Either way is correct. The output of a gate can be chained – output can be used as input for another gate. To avoid confusion when drawing circuits, a "bump" is used whenever input lines cross.

Example 1: Construct circuits that produce the following outputs:

a) $x \cdot y + \bar{x} \cdot y$

b) $(x + y + z) \cdot (\bar{x} \cdot \bar{y} \cdot \bar{z})$

Sum of Products Expansion

Suppose we are given a table of all possible values of a Boolean function. Based on those values, we can construct a Boolean expression that represents the function.

Any Boolean function can be represented by a Boolean sum of Boolean products of the variables and their complements. This means that all Boolean functions can be represented using the three Boolean operators: \cdot , $+$, and $\bar{}$.

Example 1:

Find Boolean expressions that represent the functions $F(x, y, z)$ and $G(x, y, z)$, given in the table below:

x	y	z	F	G
1	1	1	0	0
1	1	0	0	1
1	0	1	1	0
1	0	0	0	0
0	1	1	0	0
0	1	0	0	1
0	0	1	0	0
0	0	0	0	0

$$F(x, y, z) = x \cdot \bar{y} \cdot z$$

$$G(x, y, z) = x \cdot y \cdot \bar{z} + \bar{x} \cdot y \cdot \bar{z}$$

Literal – a Boolean variable or its complement

Minterm – given Boolean variables x_1, x_2, \dots, x_n , it is a Boolean product $y_1 y_2 \cdots y_n$ where

$$y_i = x_i \text{ or } y_i = \bar{x}_i, \text{ where } 1 \leq i \leq n.$$

We say that a **minterm** is a product of n **literals**, one literal for each variable. It is also referred to as a Boolean product.

The minterm $y_1 y_2 \cdots y_n$ is 1 if and only if each y_i is 1, where $1 \leq i \leq n$. This occurs if and only if $x_i = 1$ when $y_i = x_i$ and $x_i = 0$ when $y_i = \bar{x}_i$.

Exercises

1. Find a Boolean expression that represents the function F given the table below:

x	y	z	F
1	1	1	0
1	1	0	1
1	0	1	1
1	0	0	0
0	1	1	1
0	1	0	0
0	0	1	0
0	0	0	0

2. Find the sum-of-products expansions of these Boolean functions:

a) $F(x, y, z) = (x + z) \cdot y$

b) $F(x, y, z) = x \cdot \bar{y}$

c) $F(x, y, z) = y \cdot \bar{z} + x$

3. Construct circuits to produce the following outputs:

a) $\bar{x} + y$

b) $\overline{(x + y)} \cdot x$

c) $x \cdot y \cdot z + \bar{x} \cdot \bar{y} \cdot \bar{z}$

d) $\overline{(\bar{x} + z)(y + \bar{z})}$